


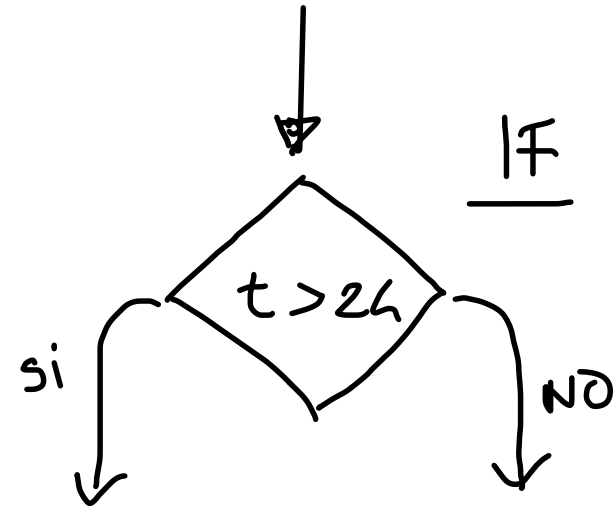


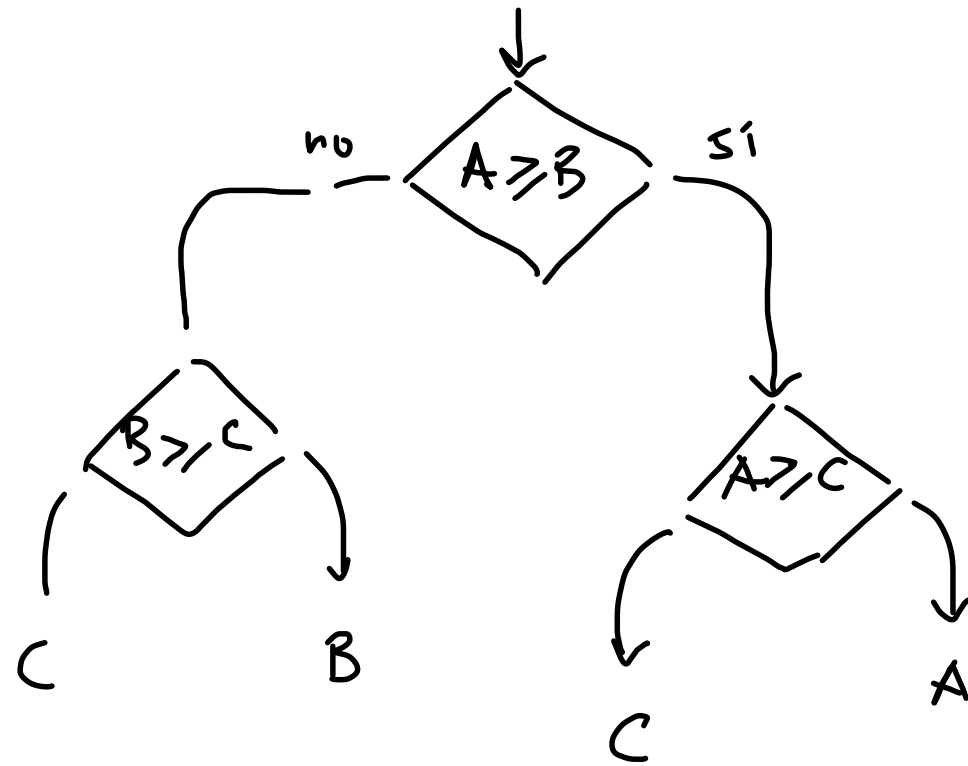


A, B, C

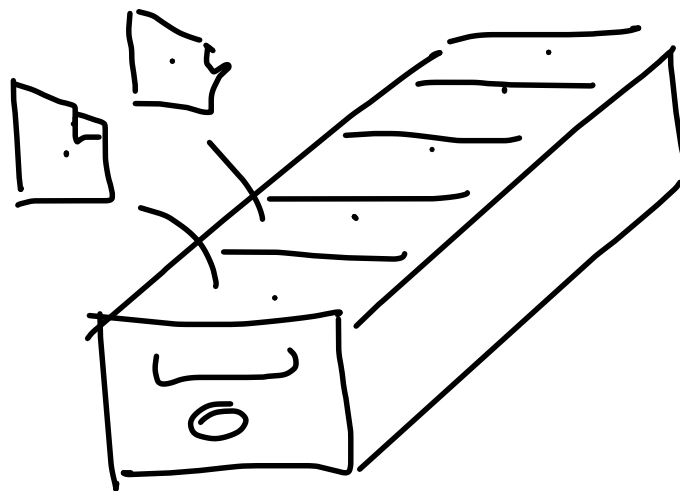

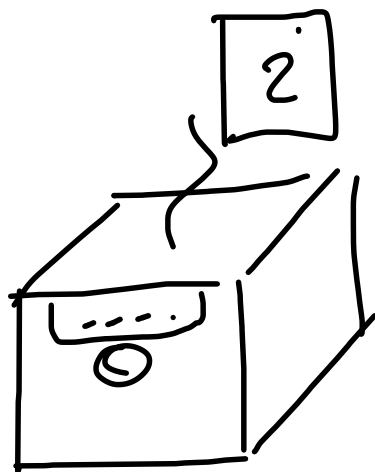


Logic boolean.

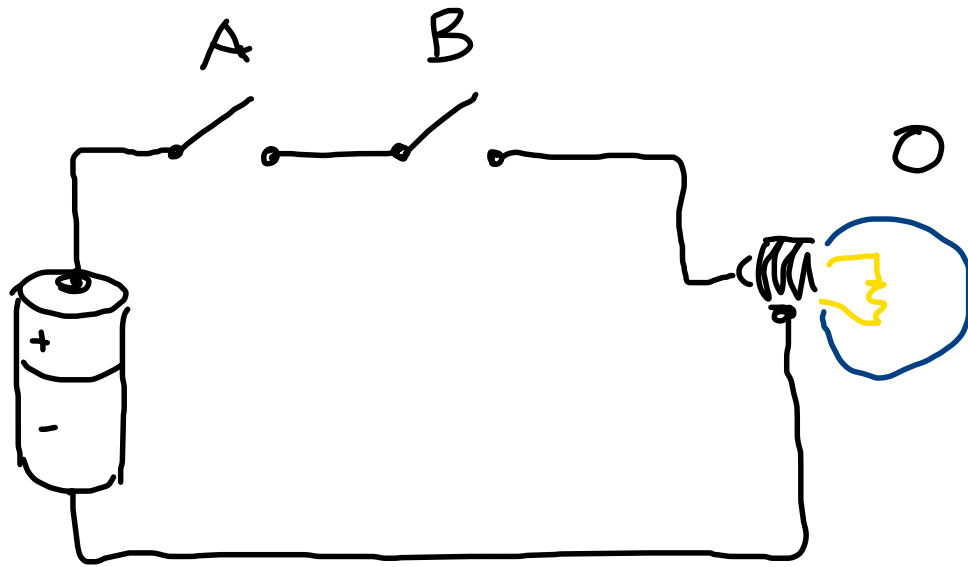



on	off
T	F
1	0

<u>AND</u>		
A	B	O
0	0	0
0	1	0
1	0	0
1	1	1

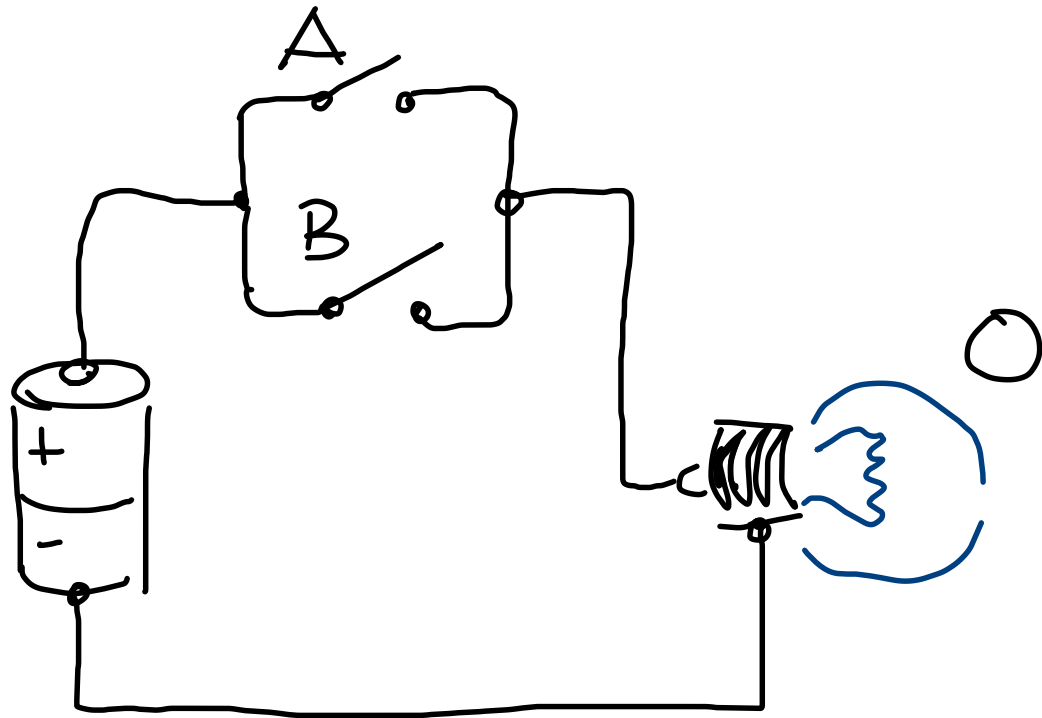

OR

A	B	O
0	0	0
0	1	1
1	0	1
1	1	1

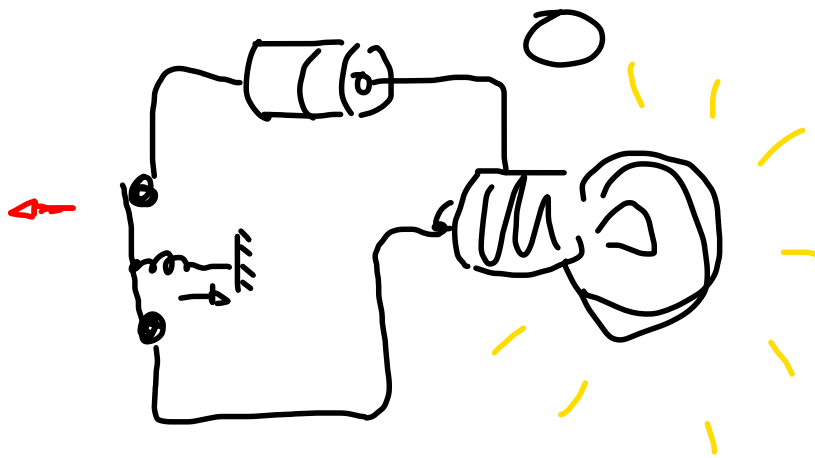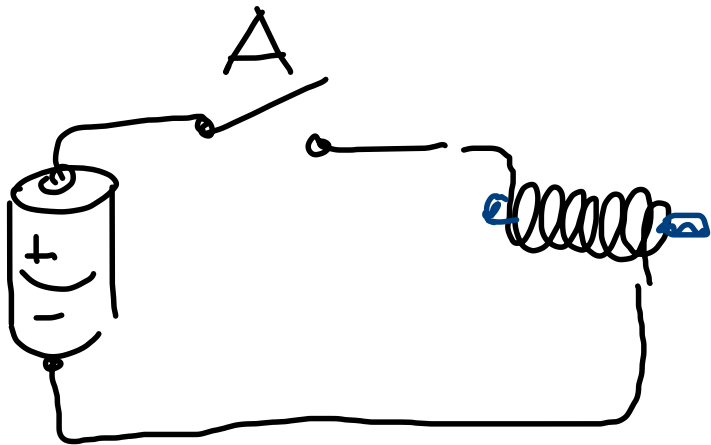

NOT

A	O
0	1
1	0

AND

OR

NOT